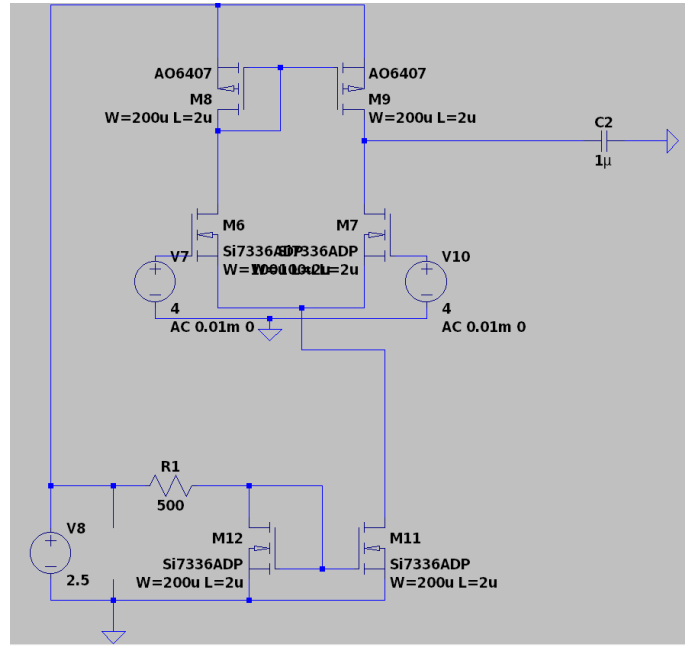


EDC Assignment 4

S A Aravind Eswar

October 1, 2025

The circuit is the following,



0.1 Small Signal Differential Gain

In simulation,

At frequency of $200mHz$ with an AC amplitude of $75\mu V$

$common\ gain = 431\mu$

$differential\ gain = 1.75k$


$CMRR = 72.3dB$

$r_o = 796k\Omega$


$g_m = 2.43m\Omega^{-1}$

Input offset voltage = 2.32V


Frequency response,

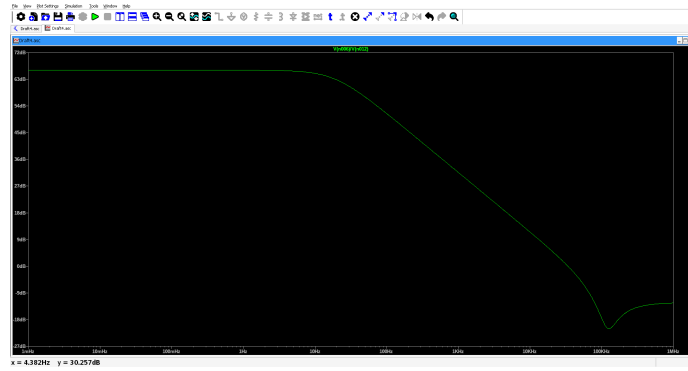

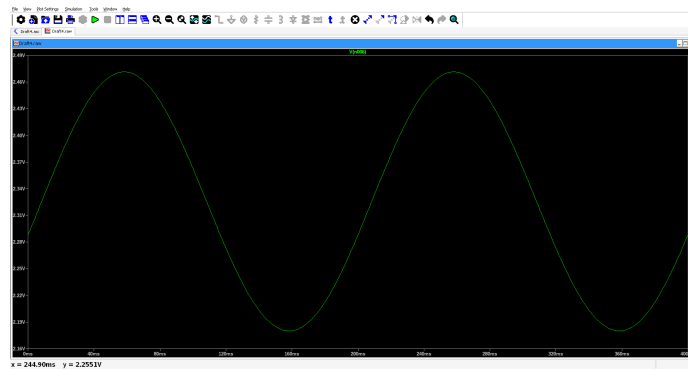
V_{out} for $V_{comm} = 4$ and $V_{diff} = 75\mu V$ sinusoid of frequency $5Hz$,



Common Mode DC Sweep,

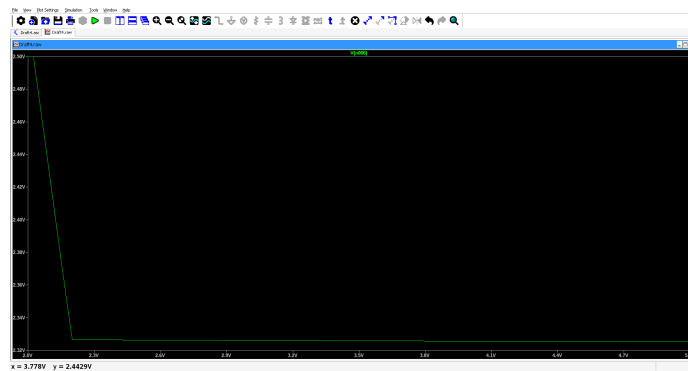

Differential Mode DC Sweep,

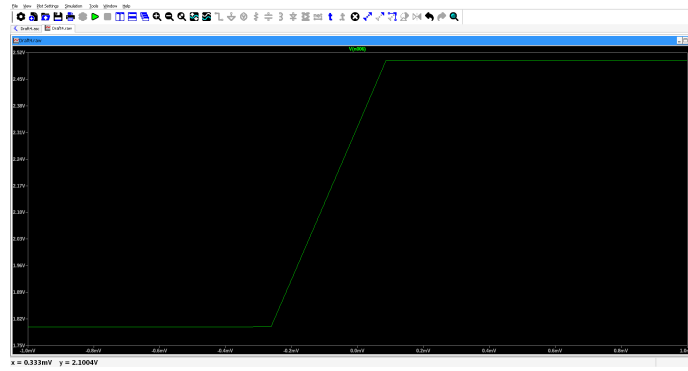

Theoretical Calculations for gain,

differential gain = $g_m(r_{on} || r_{op})$

$r_{on} = \frac{1}{\lambda I_D} = 434.8k\Omega$ $r_{op} = \infty$ as $\lambda = 0$

Thus,

$gain = 1k$

The link for the schematic (.asc file): [Link](#) (Launch with LTSpice)