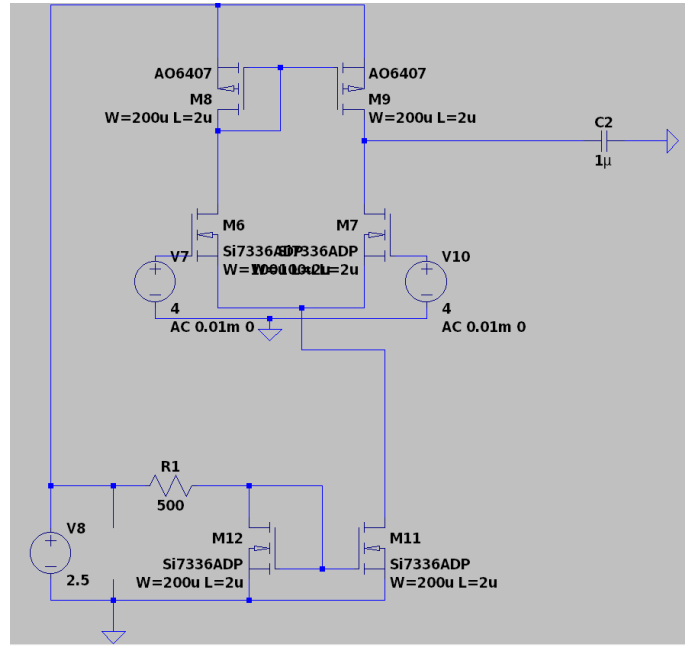


# EDC Assignment 4

S A Aravind Eswar

October 1, 2025

The circuit is the following,



## 0.1 Small Signal Differential Gain

In simulation,

At frequency of  $200\text{mHz}$  with an AC amplitude of  $75\mu\text{V}$

$\text{common gain} = 431\mu$

$\text{differential gain} = 1.75k$


$\text{CMRR} = 72.3\text{dB}$

$r_o = 796k\Omega$


$g_m = 2.43\text{m}\Omega^{-1}$

Input offset voltage =  $2.32\text{V}$


Frequency response,

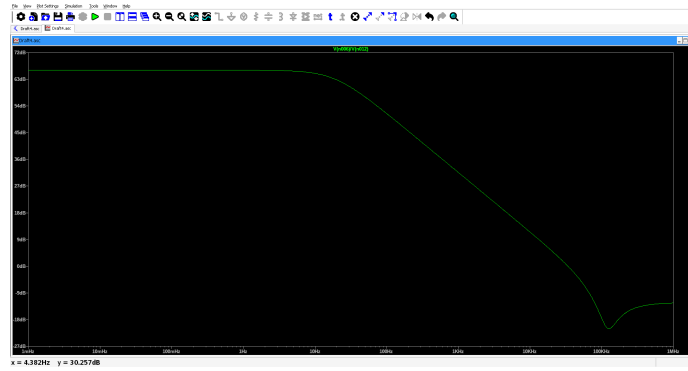

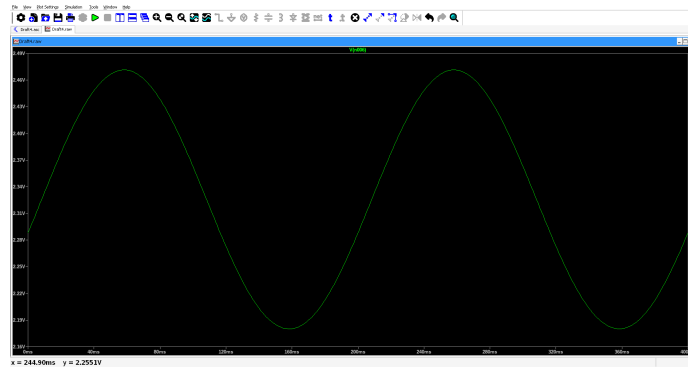
$V_{out}$  for  $V_{comm} = 4$  and  $V_{diff} = 75\mu V$  sinusoid of frequency  $5Hz$ ,



Common Mode DC Sweep,

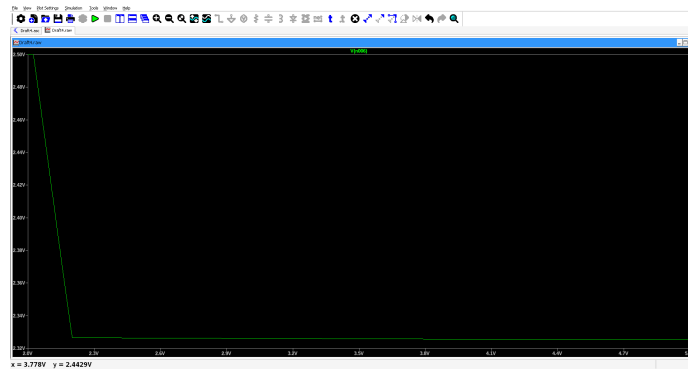

Differential Mode DC Sweep,

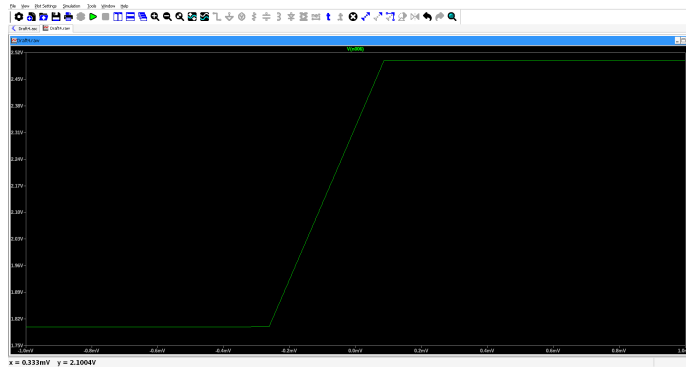

Theoretical Calculations for gain,  
differential gain =  $g_m(r_{on} || r_{op})$   
 $r_{on} = \frac{1}{\lambda I_D} = 434.8k\Omega$   $r_{op} = \infty$  as  $\lambda = 0$   
Thus,  
 $gain = 1k$